

Lava: Hardware Design in Haskell

Michael Christensen

Alvin Glova

CS595E

01/13/2021

Outline

- Considerations
- Lava HDL Introduction
- A Little about Haskell
- Lava Language
- Circuit Examples and Demos
 - Simulation
 - VHDL Code Generation
 - Verification
- Lava Families

Questions to Consider

Consider the following when picking an HDL:

- What level of abstraction is being described?
- How are circuits modelled? Shallow or deep embedding?
- What kind of data can travel through your circuits/functions?
- How will you represent sequential logic?
- What components/basic components are allowed? How to represent them?
- How will you model check it?
- How will you simulate it?
- How does lowering occur? What ops are supported?
- Will you expose the clock? Multiple clocks? Allow asynchronity?

Lava

- Family of Haskell-hosted EDSLs for expressing gate-level hardware descriptions
- These circuit descriptions that can be interpreted in several ways
 - Description
 - Simulation
 - Verification
 - Code generation
- Using Haskell
 - Take advantage of polymorphism, higher-order functions, typeclasses, purity
 - Extensible
- Control low-level details with nice functional abstractions
- Influential ancestors include μ FP and Ruby¹, and directly influenced derivatives like Kansas, Xilinx Lava, and functional HDLs

¹Probably not the Ruby you're thinking of

A Little About Haskell

- Statically-typed, HM-based, type-inferred, focus on purity
- Functions, recursion **everywhere**
- Polymorphism (`map :: (a -> b) -> [a] -> [b]`)
- `data` for creating ADTs (data structures)
- `type` for type synonyms (typedefs)
- `class` for type classes, subclassing (i.e. interfaces)
- Monads (abstract datatype of actions)
 - Often used for allowing computations to implicitly carry additional data and sequence computations in special ways (i.e. state, IO, nondeterminism, failure, etc.)

Lava Language (according to the paper)

- `Circuit` type class
- Type class hierarchy for several interpretations, enable certain operations
 - `Circuit`
 - `Arithmetic`
 - `Symbolic`
 - `Layout`
- Composition (\Rightarrow)

```
class Monad m  $\Rightarrow$  Circuit m where  
  and2, or2 :: (Bit, Bit)  $\rightarrow$  m Bit
```

```
class Circuit m  $\Rightarrow$  Arithmetic m where  
  plus, times :: (NumSig, NumSig)  $\rightarrow$  m NumSig
```

```
class Circuit m  $\Rightarrow$  Sequential m where  
  delay :: Bit  $\rightarrow$  Bit  $\rightarrow$  m Bit  
  loop :: (Bit  $\rightarrow$  m Bit)  $\rightarrow$  m Bit
```

```
class Circuit m  $\Rightarrow$  Symbolic m where  
  newBitVar :: m Bit  
  newNumVar :: m NumSig
```



```
class Circuit m  $\Rightarrow$  Layout m where  
  row :: ...  
  column :: ...
```

Chalmers Lava

- Signal type
 - `Bit ≡ Signal Bool`
 - `Binary number ≡ [Signal Bool]` (element 0 is LSB)
 - `low :: Signal Bool`
 - `high :: Signal Bool`
 - `99 :: Signal Int`
- Circuits are just functions from input (tuple of wires) to output (tuple of wires)
 - `and2 :: (Lava.Signal Bool, Lava.Signal Bool) -> Lava.Signal Bool`
 - For simulation, each input and output must be an instance of the `Generic` typeclass



Connection Patterns

- Higher order functions that capture common ways of plugging circuits together
 - Serial (\rightarrow -)
 - `serial c1 c2 = c1 . c2`
 - Compose
 - `compose cs = foldl1 (\rightarrow -) id cs`
 - Par ($-|-$)
 - `par c1 c2 (a, b) = (c1 a, c2 b)`
 - Par1
 - `par1 c1 c2 = halveList \rightarrow - (c1 $-|-$ c2) \rightarrow - append`

  

Circuit Examples and Simulation

Comb. Circuit Example: Half Adder

  

Code:

```
halfAdd :: (Signal Bool,Signal Bool) ->      type signature
      (Signal Bool,Signal Bool)              (inferred
halfAdd (a, b) = (sum, carry)                 automatically)
  where
    sum = Lava.xor2 (a,b)
    carry = Lava.and2 (a,b)
```

order does not
matter inside
"where"

Notes:

A->B: a function with input of type A and output of type B

(A1, A2): a pair allows several signals to be grouped together

Simulation


Combinational:

```
simulate :: Generic b => (a -> b) -> a -> b
```

Sequential:

```
simulateSeq :: (Generic a, Generic b) => (a -> b) -> [a] -> [b]
```

 Comb. Circuit Example: Half Adder (Simulation)




```
main> Lava.simulate halfAdd (Lava.high, Lava.low)  
(high, low)
```

```
main> Lava.simulate halfAdd (Lava.high, Lava.high)  
(low, high)
```

```
main> Lava.simulateSeq halfAdd Lava.domain  
[(low,high), (low,low), (high,low), (high,low),  
(low,high)]
```

Full Adder

 


Code

```
fullAdd (cin, (a, b)) = (sum, cout)
  where
    (sum1, carry1) = halfAdd (a, b)
    (sum, carry2)  = halfAdd (cin, sum1)
    cout          = Lava.xor2 (carry2, carry1)
```

Generating N-bit Adder from Full Adder

Recursion of Lists

 

```
adder :: (Bit, ([Bit], [Bit])) -> ([Bit], Bit)
adder (cin, ([], [])) = ([], cin)
adder (cin, (a:as, b:bs)) = (sum:sums, cout)
  where
    (sum, carry) = fullAdd (cin, (a, b))
    (sums, cout) = adder (carry, (as, bs))
```

Notes:

[A]: lists of values of type A. Examples of lists:

[] (empty list)

[low,high,low,low] :: [Bit]


[(low,high),(low,low)] :: [(Bit,Bit)]

List are used both for sequences in time and for parallel signals (busses).


Length can be arbitrary and is not indicated in the type

Generating N-bit Adder from Full Adder

Using Connection Pattern

 
 
```
serial circ1 circ2 a = c
where
  b = circ1 a
  c = circ2 b
```



```
row circ (carryIn, []) = ([], carryIn)
row circ(carryIn, a:as) = (b:bs, carryOut)
where
  (b, carry) = circ(carryIn, a)
  (bs, carryOut) = row circ (carry, as)
```

Simpler Way: N-bit Adder using row Connection Pattern

```
adder' :: (Bit, [(Bit, Bit)]) -> ([Bit], Bit)
adder' = Lava.row fullAdd
```

Sequential Circuits

Delay Component

```
delay init s
```

- delays the signal **s** by one time unit
- The output during the first time unit is **init**

```
edge inp = change
```

```
where
```

```
inp' = delay low inp
```

```
change = Lava.xor2(inp, inp')
```

```
main> Lava.simulateSeq edge [high, low, low, high]  
[high, high, low, high]
```

```
toggle change = out
```

```
where
```

```
out' = delay low out
```

```
out = Lava.xor2(change, out')
```

```
main> Lava.simulateSeq toggle [high, low, low, high]  
[high, high, high, low]
```


Sequential Circuits

n-bit Counter

Output n-bit binary number at every clock cycle (from 0, +1 every clock cycle)

```
counter n () = number'
  where
    number'          = Lava.delay (Lava.zeroList n) number
    (number, carryOut) = adder (Lava.high, (Lava.zeroList n, number'))
```

```
main> Lava.simulateSeq (counter 3) (replicate 10 ()) |> print
[[low,low,low],[high,low,low],[low,high,low],[high,high,low],[low,low,
high],[high,low,high],[low,high,high],[high,high,high],[low,low,low],[
high,low,low]]
```

LSB first

Sequential Circuits

Sequential Adder

```
adderSeq (a,b) = sum
  where
    carryIn          = delay low carryOut
    (sum, carryOut)   = fullAdd (carryIn, (a,b))

main> Lava.simulateSeq adderSeq [(high, low),
  (high, high), (low, high)]
[high, low, low]
```

Sequential Adder via rowSeq

```
adderSeq' = rowSeq fullAdd
```


Connection Patterns

- Row

- $\text{row} :: ((c, a) \rightarrow (b, c)) \rightarrow (c, [a]) \rightarrow ([b], c)$
- Connect an instance of a circuit's output to another instance's input, in sequence
- Internally, it's like a fold in purely functional terms

- RowSeq

 
- Builds a row of circuits, interpreting the row over time




Other Connection Patterns

`row (combinational)`

`rowSeq (sequential)`

 



`->- (serial composition)`

 

Combining patterns:

`map f ->- map g = map (f ->- g)`

`map`

  

Many other available:

- column
- grid
- compose
- par
- red
- lin
- tri
- etc.

Code Generation and Verification

VHDL Generation

Constructive typeclass

```
class Generic a => Constructive a
where
  zero    :: a
  var     :: String -> a
  random  :: Rnd -> a
```

Generic typeclass

```
class Generic a where
  struct    :: a -> Struct Symbol
  construct :: Struct Symbol -> a
```

VHDL netlist generation only supports
bit-level operations

VHDL Generation

Code

```
Main> Lava.writeVhdlInputOutput "4BitAdder" adder
      (Lava.var "cin", (Lava.varList 4 "a", Lava.varList 4 "b"))
      (Lava.varList 4 "sum", Lava.var "cout")
```

VHDL

```
use work.all;
entity
  4BitAdder
is
  port
    -- clock
    ( clk : in bit

    -- inputs
    ; cin : in bit
    ; a_0 : in bit
    ; a_1 : in bit
    ...
    -- outputs
    ; sum_0 : out bit
    ; sum_1 : out bit
    ...
end entity 4BitAdder;

architecture
  structural
of
  4BitAdder
is
  signal w1 : bit;
  signal w29 : bit;
begin
  c_w2  : entity id    port map (clk, cin, w2);
  c_w4  : entity id    port map (clk, a_0, w4);
  c_w5  : entity id    port map (clk, b_0, w5);
  c_w3  : entity xor2  port map (clk, w4, w5, w3);
  c_w1  : entity xor2  port map (clk, w2, w3, w1);
  c_w8  : entity and2  port map (clk, w2, w3, w8);
  ...
  c_sum_2 : entity id    port map (clk, w13, sum_2);
  c_sum_3 : entity id    port map (clk, w20, sum_3);
  c_cout  : entity id    port map (clk, w27, cout);
end structural;
```

Verification

Checkable typeclass, Property type synonym, ProofResult data type

```
class Checkable a where
  property :: a -> Property

newtype Property
  = P (Gen ([Signal Bool], Model -> [[String]]))

data ProofResult
  = Valid
  | Falsifiable
  | Indeterminate
deriving (Eq, Show)
```


Verification

SAT-Solver (minisat) / Model Checking (smv via nusmv)

```
minisat :: Checkable a => a -> IO ProofResult
minisat a =
  do checkVerifyDir
     noBuffering
     (props,_) <- properties a
     proveFile defsFile (writeDefinitions defsFile props)
```

Verification tool wrappers

- Captain
- Eprover
- HeerHugo
- ISC
- Limmat
- **Minisat** (minisat) SAT solver
- Modoc
- Satnik
- Satzoo
- **SMV** (nusmv) model checker
- Vis
- Zchaff

Verification (using minisat)

```
prop_HalfAddOutputNeverBothTrue (a, b) = ok
  where
    (sum, carry) = halfAdd (a, b)
    ok           = Lava.nand2 (sum, carry)
```

```
prop_FullAddCommutative (c, (a, b)) = ok
  where
    out1 = fullAdd (c, (a, b))
    out2 = fullAdd (c, (b, a))
    ok = out1 Lava.<==> out2
```

```
main> Lava.minisat
      prop_HalfAddOutputNeverBothTrue
      >>= print
```

```
Minisat: ...
real      0m0.011s
user      0m0.001s
sys       0m0.002s
(t=) Valid.
Valid
```

Verification (using nusmv)

```
prop_SameAdderSeq inp = ok
  where
    out1 = adderSeq inp
    out2 = adderSeq' inp
    ok    = out1 Lava.<==> out2
```

```
main> Lava.smv prop_SameAdderSeq >>= print
```

```
Smv: ...
real      0m0.059s
user      0m0.005s
sys       0m0.009s
(t=) Valid.
Valid
```

Compare to simulation over all inputs:

```
main > Lava.simulateSeq
prop_SameAdderSeq Lava.domain
```

```
[high,high,high,high]
```

Questions to (Re)Consider

Consider the following when picking an HDL:

- What level of abstraction is being described?
- How are circuits modelled? Shallow or deep embedding?
- What kind of data can travel through your circuits/functions?
- How will you represent sequential logic?
- What components/basic components are allowed? How to represent them?
- How will you model check it?
- How will you simulate it?
- What can be generated? How does lowering occur? What ops are supported?
- Will you expose the clock? Multiple clocks? Allow asynchronicity?

Personal Experience

Good things

- Access to all of Haskell's combinators and libraries
- Focus on verifiability with wrappers for external solvers/model checkers

Limitations


- Having to distinguish between `Signal Bool` and `Signal Int`
- Hard to synthesize custom data types (e.g. enum for mux control)
 - **What is simulatable is not always synthesizable**
- Uncurrying inputs/outputs (circuits are `(a -> b)`)
- List don't enforce size constraints

Lava Families

- Chalmers Lava (focus of this presentation)...
- Kansas Lava
 - `Signal` type (an applicative functor) for all types of signals (now in Chalmer's Lava)
 - Direct support for including existing VHDL libraries as primitives
 - Type functions to implement sized types
- York Lava
 - Recipes, RAMs, no model checking
- Xilinx Lava
 - Extra modules used for FPGA layout and hardware verification
 - Direct way to specify the mapping into CLB, slices and LUT
 - [Tutorial and examples](#)
- Cava
 - Coq-based Lava (theorem prover)

The End

<https://github.com/pllab/Lava-Testing>

 

References

- Satnam Singh's LAVA Resources:
 - <https://fpcastle.com/lava/>
- Chalmers University TDA956 Course site:
 - <http://www.cse.chalmers.se/edu/year/2012/course/TDA956/>
- Per Bjesse, Koen Claessen, Mary Sheeran, and Satnam Singh. 1998. **Lava: hardware design in Haskell**. In Proceedings of the third ACM SIGPLAN international conference on Functional programming (ICFP '98). Association for Computing Machinery, New York, NY, USA, 174–184.
- Gill A., Bull T., Kimmell G., Perrins E., Komp E., Werling B. (2010) **Introducing Kansas Lava**. In: Morazán M.T., Scholz SB. (eds) Implementation and Application of Functional Languages. IFL 2009. Lecture Notes in Computer Science, vol 6041. Springer, Berlin, Heidelberg.
https://doi.org/10.1007/978-3-642-16478-1_2
- Jones G., Sheeran M. (1993) **Designing arithmetic circuits by refinement in Ruby**. In: Bird R.S., Morgan C.C., Woodcock J.C.P. (eds) Mathematics of Program Construction. MPC 1992. Lecture Notes in Computer Science, vol 669. Springer, Berlin, Heidelberg. https://doi.org/10.1007/3-540-56625-2_15
- <http://www.perbjesse.com/phd.pdf>